

7.17 In the circuit shown in the diagram the 10-volt battery has negligible internal resistance. The switch S is closed for several seconds, then opened. Make a graph with the abscissa time in milliseconds, showing the potential of point A with respect to ground, just before and then for 10 milliseconds after the opening of switch S . Show also the variation of the potential at point B in the same period of time.