

8.12 Let $V_{AB} = V_B - V_A$, in this circuit. Show that $|V_{AB}|^2 = V_0^2$ for any frequency ω . Find the frequency for which V_{AB} is 90° out of phase with V_0 .