

8.13 Show that, if the condition $R_1 R_2 = L/C$ is satisfied by the components of the circuit below, the difference in voltage between points A and B will be zero at any frequency. Discuss the suitability of this circuit as an ac bridge for measurement of an unknown inductance.