

8.10 Is it possible to find a frequency at which the impedance at the terminals of this circuit will be purely real?