

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Experimental Study Group

Physics 8.022, Spring 2011

Problem Set 10  
RLC circuits, AC circuits

Due: Wednesday, April 27th, 10 pm

Problem 1: Problem 1 Purcell 7.17

Extra question — By grounding this circuit, we make the switch safer to operate. Describe why a large spark jumps across the switch when it is not grounded, and why the spark does not happen when it is grounded.

Problem 2: Problem 2 Purcell 8.4

Problem 3: Problem 3 Purcell 8.7

A resonant cavity of the form illustrated is an essential part of many microwave oscillators. It can be regarded as a simple  $LC$  circuit. The inductance is that of a toroid with one turn. Find an expression for the resonant frequency of this circuit and show by a sketch the configuration of the magnetic and electric fields.

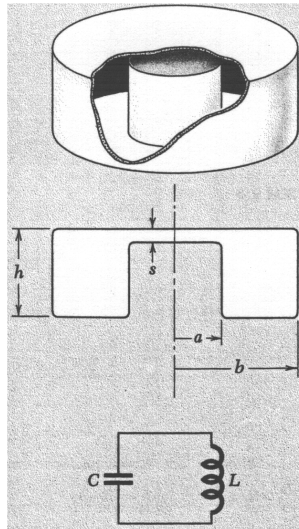


Figure 1: Purcell 8.7

**Problem 4: Problem 4 Purcell 8.9**

**Problem 5: Problem 5 Purcell 8.12**

**Problem 6: Problem 6 Purcell 8.16**

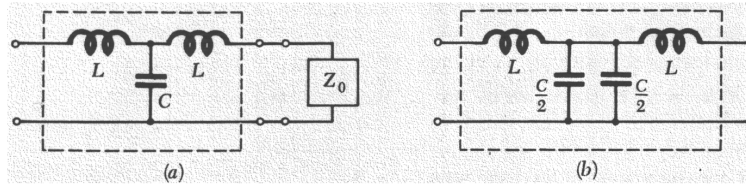


Figure 2: Purcell 8.16

An impedance  $Z_o$  is to be connected to the terminals on the right. For given frequency  $\omega$  find the value which  $Z_o$  must have if the resulting impedance between the left terminals is  $Z_o$ . The required  $Z_o$  is a pure resistance  $R_o$  provided  $\omega^2 < 2/LC$ . What is  $Z_o$  in the special case  $\omega = \sqrt{2/LC}$ ?

**Problem 7: Problem 7 – Optional Purcell 8.10**

**Problem 8: Problem 8 – Optional Purcell 8.13**

**Problem 9: Problem 9 – Optional Purcell 8.14**