

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Experimental Study Group

Physics 8.022, Spring 2011

Problem Set 10 Solutions  
RLC circuits, AC circuits


Due: Wednesday, April 27th, 10 pm

Problem 1: Purcell 7.17

Problem

**7.17** In the circuit shown in the diagram the 10-volt battery has negligible internal resistance. The switch  $S$  is closed for several seconds, then opened. Make a graph with the abscissa time in milliseconds, showing the potential of point  $A$  with respect to ground, just before and then for 10 milliseconds after the opening of switch  $S$ . Show also the variation of the potential at point  $B$  in the same period of time.

Figure 1: Purcell 7.17

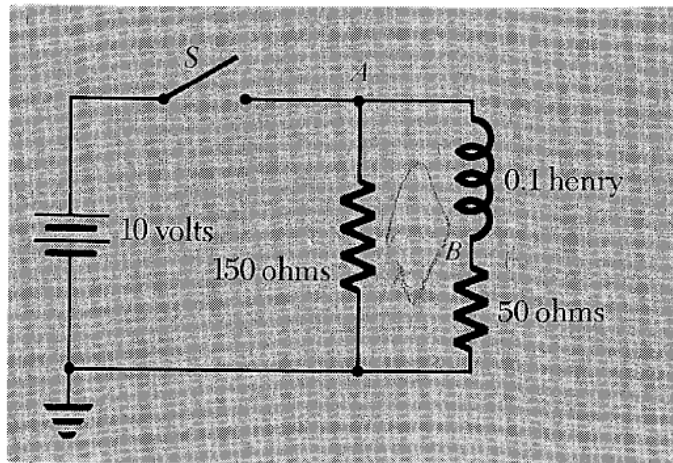

**PROBLEM 7.17**

Figure 2: Figure Purcell 7.17

Extra question — By grounding this circuit, we make the switch safer to operate. Describe why a large spark jumps across the switch when it is not grounded, and why the spark does not happen when it is grounded.

# Solution

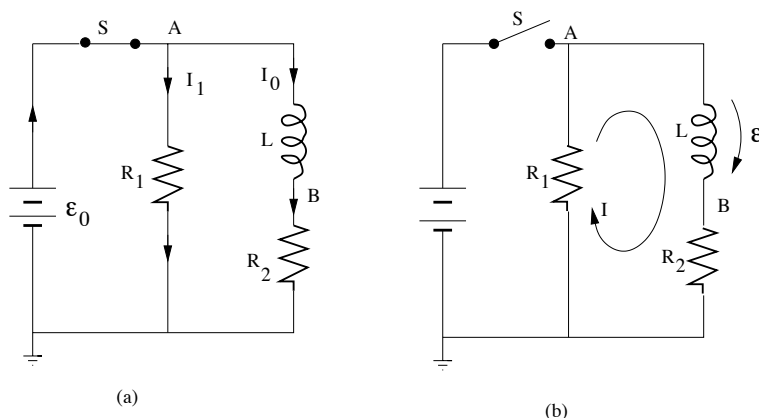


Figure 3: LR circuit: (a) steady state when switch S has been closed for a long time; (b) the current in LR circuit when switch S is opened.

Note: we'll use SI unit in this problem for convenience; and below  $\mathcal{E}_0 = 10 \text{ volts}$ ,  $R_1 = 150 \text{ ohms}$ ,  $R_2 = 50 \text{ ohms}$ ,  $L = 0.1 \text{ henry}$ .

Switch S is closed (see Figure 3a) for several seconds, which is long enough that the current in the inductor is steady; hence the EMF due to the inductor  $\mathcal{E} = 0$ . Right right before S is opened, the current on L is  $I_0 = \mathcal{E}_0/R_2 = 0.2 \text{ amp}$ . The potential of point A with respect to ground is, for  $t < 0$ ,  $V_A = \mathcal{E}_0 = 10 \text{ volts}$ ; and the potential of point B is, for  $t < 0$ ,  $V_B = I_0 R_2 = \mathcal{E}_0 = 10 \text{ volts}$ .

After switch S has been opened (Figure 3b), current will decay in the loop containing  $L$ ,  $R_2$  and  $R_1$ , and the change in current induces an electromotive force  $\mathcal{E}$  on the inductor. Define the positive electromotive force and positive current as shown in Figure 3b; under this convention, they satisfy  $\mathcal{E} = -L \frac{dI}{dt}$ . Apply Kirchhoff's rule,

$$-\mathcal{E} + I(R_1 + R_2) = 0. \quad (1)$$

A simple calculation gives an ordinary differential equation for I:

$$L \frac{dI}{dt} = -(R_1 + R_2)I. \quad (2)$$

The solution of eq.(2) with initial condition  $I(t = 0) = I_0$  is, for  $t > 0$ ,

$$I(t) = I_0 e^{-t/\tau}, \quad (3)$$

$$\text{where } \tau = L/(R_1 + R_2) = 0.5 \text{ milliseconds}. \quad (4)$$

The potentials of point A and point B with respect to ground are, for  $t > 0$

$$V_A = -I(t)R_1 = -I_0 R_1 e^{-t/\tau} = -30 e^{-t/0.5} \text{ volts}; \quad (5)$$

$$V_B = I(t)R_2 = I_0 R_2 e^{-t/\tau} = 10 e^{-t/0.5} \text{ volts}, \quad (6)$$

where  $t$  is in milliseconds. The plots of potentials Vs. time are shown in Figure 7.

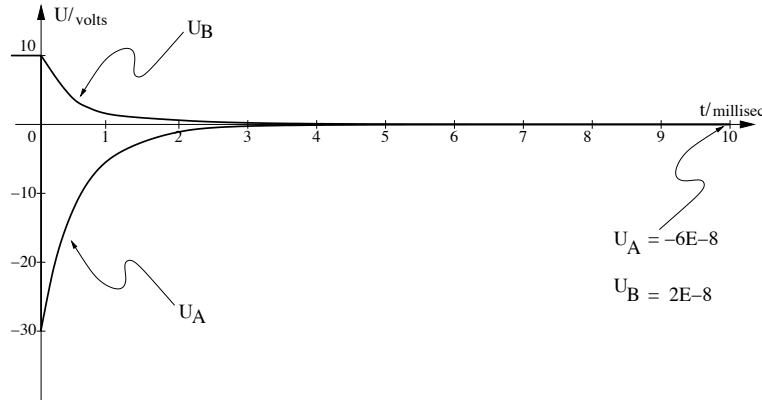


Figure 4: The exponential decay of the potentials in the LR circuit. At  $t < 0$ , both  $V_A$  and  $V_B$  are at 10 volts; at  $t = 0$ ,  $V_A$  abruptly drops to -30 volts, while  $V_B$  is continuous.

Additional question:

Notice that the current in the 150 Ohm resistor has to abruptly switch magnitude and direction at the moment that the switch is opened. If the circuit were not grounded, the only way to suddenly change the direction of the current would be to “suck” the current needed to maintain continuity over from the battery – zap!

Ground fixes this: we can think of ground as an infinite sink or source of charge, and hence of current. By sucking (or dumping) the current needed from ground, the current in the 150 Ohm resistor can switch directions very rapidly – there is no need for a big zap across the switch.

## Problem 2: Purcell 8.4

### Problem

**8.4** In the resonant circuit of the figure the dissipative element is a resistor  $R'$  connected in parallel, rather than in series, with the  $LC$  combination. Work out the equation, analogous to Eq. 2, which applies to this circuit. Find also the conditions on the solution analogous to those that hold in the series  $RLC$  circuit. If a series  $RLC$  and a parallel  $R'LC$  circuit have the same  $L$ ,  $C$ , and  $Q$ , how must  $R'$  be related to  $R$ ?

Figure 5: Purcell 8.04

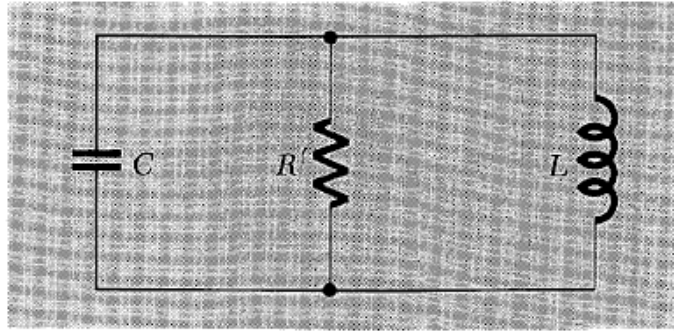

**PROBLEM 8.4**

Figure 6: Purcell 8.04

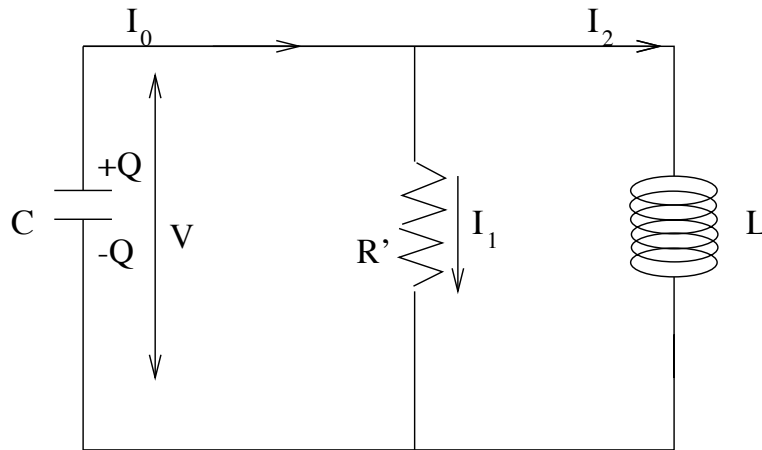
**Solution**


Figure 7: RLC circuit

If  $V=Q/C$  is the voltage drop across the capacitor, then Kirchoff's laws for the left and right-hand loops above give:

$$V - I_1 R' = 0 \quad (7)$$

$$-L \frac{dI_2}{dt} + I_1 R' = 0 \quad (8)$$

$$I_0 = I_1 + I_2 \quad (9)$$

We also know that  $I_0 = -dQ/dt$  and that  $Q=CV$ , so we can write

$$I_0 = -C \frac{dV}{dt} \quad (10)$$

The first Kirchoff equation gives us  $I_1 = V/R'$ . The derivative  $dI_2/dt$  in the second equation can be written:

$$\frac{dI_2}{dt} = \frac{d(I_0 - I_1)}{dt} = \frac{dI_0}{dt} - \frac{dI_1}{dt} = -C \frac{d^2 V}{dt^2} - \frac{1}{R'} \frac{dV}{dt} \quad (11)$$

Thus we can rewrite the second Kirchoff equation as a differential equation for  $V$ :

$$\frac{d^2V}{dt^2} + \left(\frac{1}{CR'}\right) \frac{dV}{dt} + \left(\frac{1}{LC}\right) V = 0 \quad (12)$$

Compare this to the differential equation for  $V$  in the case of a serial LRC circuit, Purcell, Ch.8, eq.(2).

$$\frac{d^2V}{dt^2} + \left(\frac{R}{L}\right) \frac{dV}{dt} + \left(\frac{1}{LC}\right) V = 0 \quad (13)$$

Thus the solution to equation (12) can be read off directly from the solution to equation (13) (i.e. the discussion following eq.(2) of Purcell Ch.8) by the substitution

$$R \rightarrow \frac{L}{R'C} \quad (14)$$

$$\text{and in particular} \quad \alpha = \frac{R}{2L} \rightarrow \alpha' = \frac{1}{2R'C} \quad (15)$$

Analogous to the serial RLC, the oscillation frequency is real and hence the solution oscillates when  $\alpha' < \omega_0 = 1/\sqrt{LC}$ ; this means we must have

$$R' > \frac{1}{2} \sqrt{\frac{L}{C}} \quad (16)$$

When the parallel and serial circuits have the same  $L, C$ , and quality factor  $Q$  (not to be confused with the charge on the capacitor), we want to find a relation between  $R'$  and  $R$ . Recall that the quality factor for the serial RLC may be written

$$Q = \frac{\omega}{2\alpha} = \frac{\sqrt{\omega_0^2 - \alpha^2}}{2\alpha} \quad (17)$$

Thus  $Q$  for the parallel RLC

$$Q' = \frac{\sqrt{\omega_0^2 - \alpha'^2}}{2\alpha'} \quad (18)$$

Clearly  $Q' = Q$  implies that  $\alpha' = \alpha$ , or  $R' = L/RC$ .

## Problem 3: Purcell 8.7

### Problem

A resonant cavity of the form illustrated is an essential part of many microwave oscillators. It can be regarded as a simple  $LC$  circuit. The inductance is that of a toroid with one turn. Find an expression for the resonant frequency of this circuit and show by a sketch the configuration of the magnetic and electric fields. Hint: the capacitor is composed by the upper and lower disks

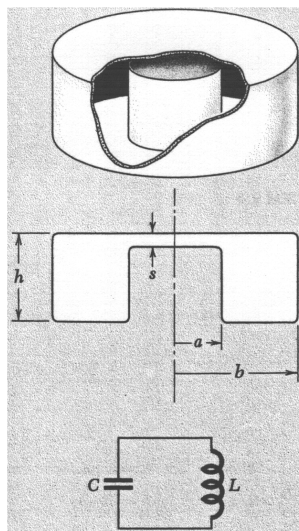


Figure 8: Purcell 8.7

## Solution

The resonant cavity is equivalent to a simple LC circuit. The inductor is a configuration of currents uniformly flowing up and down on the surface of the inner conducting cylinder and the outer one. The capacitor is a pair of parallel plates of separation  $s$  and area  $A = \pi a^2$ . Quote the result in Problem 8 of pset 8: the inductance *per unit length* is

$$L/l = \frac{2}{c^2} \ln\left(\frac{b}{a}\right).$$

This gives the total inductance

$$L = (h - s) \frac{2}{c^2} \ln\left(\frac{b}{a}\right).$$

[You could also use Purcell (58) of Chapter 7; you would get  $h$  in place of  $h - s$ , which is good enough for small  $s$ .]

The capacitor is  $C = A/4\pi s = a^2/4s$ . So the resonant frequency is

$$\omega_0 = \frac{1}{\sqrt{LC}} = \left( \frac{a^2(h - s)}{2sc^2} \ln\left(\frac{b}{a}\right) \right)^{-1/2} \approx \left( \frac{a^2h}{2sc^2} \ln\left(\frac{b}{a}\right) \right)^{-1/2}. \quad (19)$$

The configuration of the electric and magnetic field is shown in Figure 9.

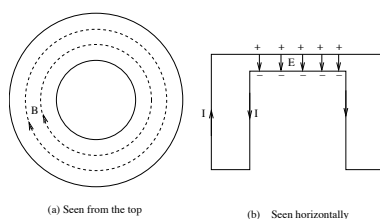


Figure 9: The configuration of  $\vec{B}$  (a) and  $\vec{E}$  field (b). The magnetic field lines are circles between the inner and the outer cylinders. The electric field lines are parallel straight lines between the top plates.

## Problem 4: Purcell 8.9

### Problem

**8.9** Using Eqs. 10 and 13, express the effect of damping on the frequency of a series  $RLC$  circuit. Let  $\omega_0 = 1/\sqrt{LC}$  be the frequency of the undamped circuit. Suppose enough resistance is added to bring  $Q$  from  $\infty$  down to 1000. By what percentage is the frequency  $\omega$  thereby shifted from  $\omega_0$ ?

Figure 10: Purcell 8.09

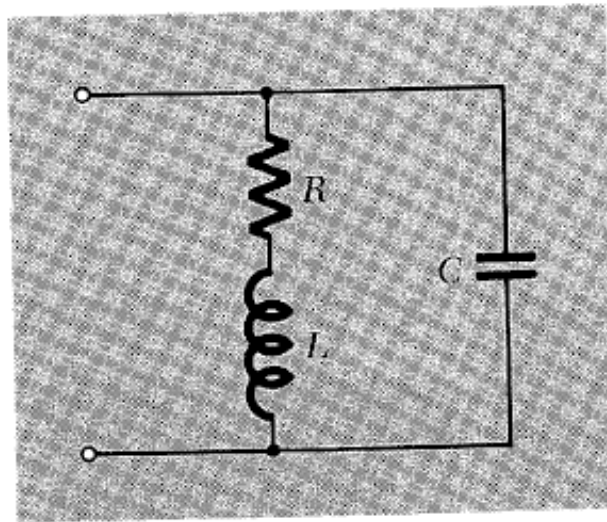


Figure 11: Purcell 8.09

### Solution

Use eqs.(13) or (14) of Purcell p.301-302.

$$R = \frac{\omega L}{Q} \quad \rightarrow \quad \frac{R}{L} = \frac{\omega}{Q}. \quad (20)$$

Plug this into eq.(10) of Purcell p.299.

$$\omega^2 = \omega_0^2 - \frac{\omega^2}{4Q^2}, \quad (21)$$

$$\text{so } \omega = \omega_0 \left( 1 + \frac{1}{4Q^2} \right)^{-1/2} \quad (22)$$

$$= \omega_0 \frac{2Q}{\sqrt{1 + 4Q^2}}. \quad (23)$$

where  $\omega_0 = 1/\sqrt{LC}$ . The percentage change is

$$\begin{aligned}
 \text{Percentage change} &= \frac{\omega_0 - \omega}{\omega_0} \times 100\% \\
 &= \left[ 1 - \left( 1 + \frac{1}{4Q^2} \right)^{-1/2} \right] \times 100\% \\
 &\approx \frac{1}{8Q^2} \times 100\% \\
 &= 1.25 \times 10^{-5}\%,
 \end{aligned} \tag{24}$$

for  $Q = 1000$ . (The binomial expansion was used to simplify the exact formula.)

## Problem 5: Purcell 8.12

### Problem

**8.12** Let  $V_{AB} = V_B - V_A$  in this circuit. Show that  $|V_{AB}|^2 = V_0^2$  for any frequency  $\omega$ . Find the frequency for which  $V_{AB}$  is  $90^\circ$  out of phase with  $V_0$ .

Figure 12: Purcell 8.12

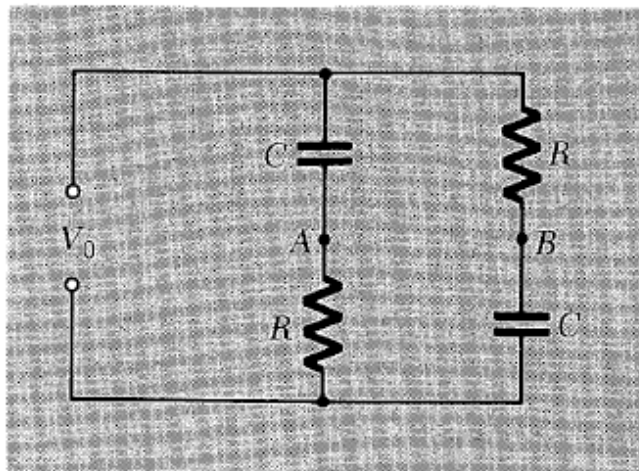


Figure 13: Purcell 8.12



## Solution

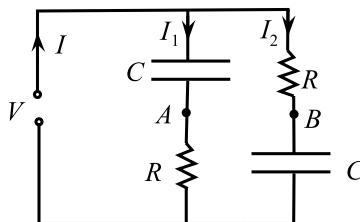


Figure 14: Circuit with resistors and capacitors

Considering the two circuit loops that contain  $V_0$ , we can find the following equations relating the currents  $I_1$  and  $I_2$  to the voltage  $V_0$ :

$$V_0 = I_1 Z_1 = I_1 \left( \frac{-i}{\omega C} + R \right) \quad V_0 = I_2 Z_2 = I_2 \left( R + \frac{-i}{\omega C} \right)$$

The voltage  $V_{AB} = V_B - V_A$  is then:

$$V_{AB} = -I_2 R + I_1 \left( \frac{-i}{\omega C} \right)$$

Substituting for the currents  $I_1$  and  $I_2$ , we find:

$$V_{AB} = -\frac{V_0 R}{R + \frac{-i}{\omega C}} + \frac{V_0 \left( \frac{-i}{\omega C} \right)}{R + \frac{-i}{\omega C}} = -V_0 \frac{R + \frac{i}{\omega C}}{R - \frac{i}{\omega C}} = V_0 \frac{1 - i\omega RC}{1 + i\omega RC}$$

We can take the absolute value of both side to get:

$$|V_{AB}|^2 = |V_0|^2 \left( \frac{1 - i\omega RC}{1 + i\omega RC} \right) \left( \frac{1 + i\omega RC}{1 - i\omega RC} \right) = |V_0|^2 \frac{1 + (RC\omega)^2}{1 + (RC\omega)^2} = |V_0|^2$$

In order for  $V_{AB}$  and  $V_0$  to be out of phase by  $\phi = -\pi/2$ , we must have

$$V_{AB} = V_0 e^{i\phi} = V_0 e^{-i\frac{\pi}{2}} = -iV_0$$

Therefore ,

$$\frac{1 - i\omega RC}{1 + i\omega RC} = -i \quad \Rightarrow \quad \frac{1 - (RC\omega)^2}{1 + (RC\omega)^2} - i \frac{2RC\omega}{1 + (RC\omega)^2} = -i$$

Equating the real parts (the imaginary parts give the same result), we find:

$$1 - (RC\omega)^2 = 0 \quad \Rightarrow \quad \omega = \frac{1}{RC}$$

## Problem 6: Purcell 8.16

### Problem

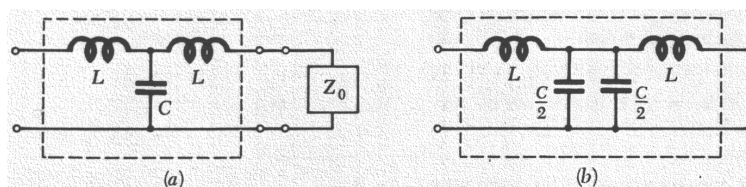


Figure 15: Purcell 8.16

An impedance  $Z_o$  is to be connected to the terminals on the right. For given frequency  $\omega$  find the value which  $Z_o$  must have if the resulting impedance between the left terminals is  $Z_o$ . The required  $Z_o$  is a pure resistance  $R_o$  provided  $\omega^2 < 2/LC$ . What is  $Z_o$  in the special case  $\omega = \sqrt{2/LC}$ ?

### Solution

We combine the impedances like resistances so that the total impedance is

$$Z = Z_L + \frac{1}{\frac{1}{Z_C} + \frac{1}{Z_L + Z_o}} ,$$

with  $Z_L = i\omega L$  and  $Z_C = 1/i\omega C$ . We set this equal to  $Z_o$  and simplify to obtain

$$Z_o = \sqrt{-\omega^2 L^2 + 2L/C} .$$

This will be pure real and thus a pure resistance if

$$-\omega^2 L^2 + 2\frac{L}{C} > 0 ,$$

$$\omega^2 < \frac{2}{LC} .$$

In the special case  $\omega = \sqrt{2/LC}$ , we have  $Z_o = 0$ .

## Problem 7: Optional Purcell 8.10

### Problem

**8.10** Is it possible to find a frequency at which the impedance at the terminals of this circuit will be purely real?

Figure 16: Purcell 8.10

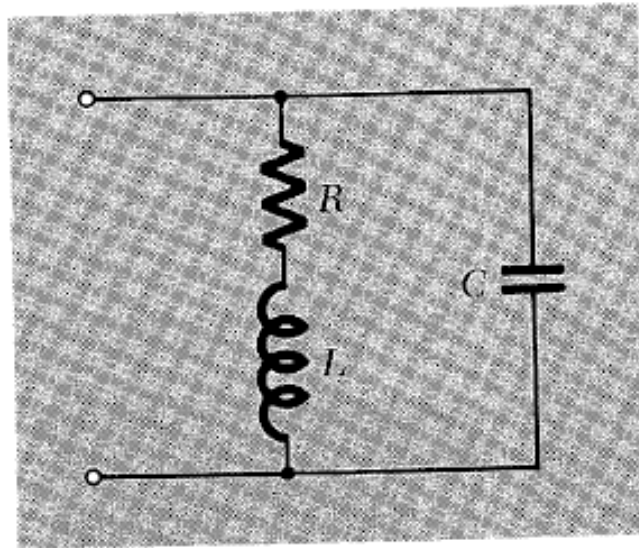


Figure 17: Purcell 8.10

### Solution

$$\begin{aligned}\frac{1}{Z} &= i\omega C + \frac{1}{R + i\omega L} \\ \frac{1}{Z} &= \left[ i\omega C + \frac{R - i\omega L}{R^2 + (\omega L)^2} \right] \\ &= \left[ i\left(\omega C - \frac{\omega L}{R^2 + (\omega L)^2}\right) + (\text{real part}) \right].\end{aligned}\quad (25)$$

To make  $Z$  purely real,  $Z^{-1}$  must be real. So

$$\omega C = \frac{\omega L}{R^2 + (\omega L)^2}, \quad (26)$$

$$\omega = \sqrt{\frac{L - CR^2}{CL^2}}. \quad (27)$$

Note that the argument inside a square root must be positive. Therefore the condition under which it is possible to find a frequency so that  $Z$  is purely real is

$$L/C > R^2. \quad (28)$$

### Problem 8: Optional Purcell 8.13

#### Problem

**8.13** Show that, if the condition  $R_1 R_2 = L/C$  is satisfied by the components of the circuit below, the difference in voltage between points  $A$  and  $B$  will be zero at any frequency. Discuss the suitability of this circuit as an ac bridge for measurement of an unknown inductance.

Figure 18: Purcell 8.13

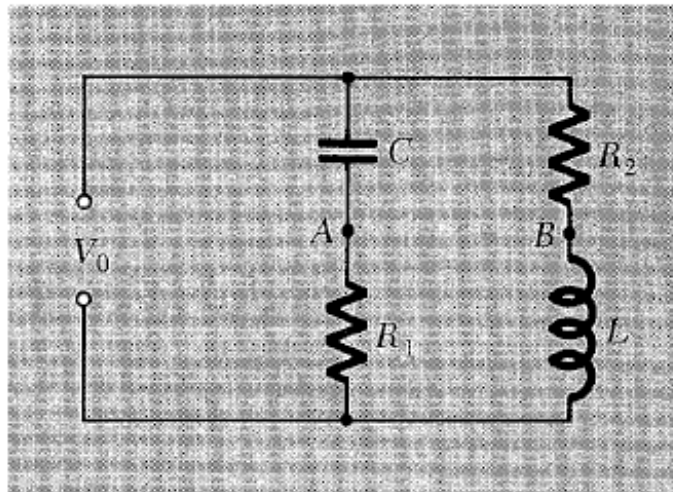


Figure 19: Purcell 8.13

## Solution

Refer to the figure for Problem 8.13 of Purcell p.321. The impedance of the left path ( $C - R_1$ ) and the right ( $R_2 - L$ ) are respectively

$$Z_1 = R_1 - \frac{i}{\omega C}, \quad Z_2 = R_2 + i\omega L.$$

Set the voltage at the bottom of the circuit to be zero. Then the voltages at the points A and B are respectively

$$\begin{aligned} V_A &= \frac{V_0}{Z_1} R_1 = \frac{V_0 R_1}{R_1 - \frac{i}{\omega C}}, \\ V_B &= \frac{V_0}{Z_2} (i\omega L) = \frac{V_0 i\omega L}{R_2 + i\omega L}. \end{aligned} \quad (29)$$

Solve  $V_A = V_B$ .

$$\begin{aligned} R_1(R_2 + i\omega L) &= i\omega L(R_1 - \frac{i}{\omega C}) \\ \text{or} \quad R_1 R_2 &= L/C. \end{aligned} \quad (30)$$

Since condition (30) doesn't depend on the value of frequency, we conclude that, if condition (30) is satisfied, the voltage difference between points A and B will be zero at any frequency.

We may employ this condition to measure unknown inductance. The circuit is exactly the same, but we connect points A and B by an AC voltmeter. The values of  $R_1$ ,  $R_2$  and  $C$  are known; at least one of the resistance should be adjustable. We then adjust the resistance so that the reading in the voltmeter vanishes. If necessary, we may adjust the frequency to check that this vanishing doesn't depend on frequency. At the vanishing point the condition (30) is satisfied and the inductance is measured by  $L = R_1 R_2 C$ .

## Problem 9: Optional Purcell 8.14

### Problem

**8.14** In the laboratory you find an inductor of unknown inductance  $L$  and unknown internal resistance  $R$ . Using a dc ohmmeter, an ac voltmeter of high impedance, a 1-microfarad capacitor, and a 1000-Hz signal generator, determine  $L$  and  $R$  as follows: According to the ohmmeter,  $R$  is 35 ohms. You connect the capacitor in series with the inductor and the signal generator. The voltage across both is 10.1 volts. The voltage across the capacitor alone is 15.5 volts. You note also, as a check, that the voltage across the inductor alone is 25.4 volts. How large is  $L$ ? Is the check consistent?

Figure 20: Purcell 8.14

### Solution

Consider the RLC in series.

$$Z_{LR} = R + i\omega L, \quad Z_c = -i/\omega C, \quad Z_{\text{total}} = R + i(\omega L - 1/\omega C). \quad (31)$$

From the potential across both and across the capacitor,

$$\frac{V_{\text{total}}}{V_C} = \frac{Z_{\text{total}}}{Z_C} = i\omega CR + (1 - \omega^2 CL), \quad (32)$$

$$\text{so} \quad \left| \frac{V_{\text{total}}}{V_C} \right| = \sqrt{(\omega CR)^2 + (1 - \omega^2 CL)^2}, \quad (33)$$

After doing some math, we find the expression for L,

$$L = \frac{1}{\omega^2 C} \left[ 1 \pm \sqrt{\left| \frac{V_{\text{total}}}{V_C} \right|^2 - (\omega CR)^2} \right] \quad (34)$$

Plug in  $\omega = 2\pi f = 2\pi \times 1000$  Hz,  $V_{\text{total}} = 10.1$  volts,  $V_C = 15.5$  volts,  $C = 10^{-6}$  farad,  $R = 35$  ohm, we get

$$L = 0.041 \text{ henry} \quad \text{or} \quad 0.0098 \text{ henry}.$$

To check the consistency, calculate the ratio

$$\frac{V_{LR}}{V_C} = \frac{Z_{LR}}{Z_C} = i\omega CR - \omega^2 CL \quad (35)$$

$$\text{so} \quad \left| \frac{V_{LR}}{V_C} \right| = \sqrt{(\omega CR)^2 + (\omega^2 CL)^2} \quad (36)$$

$$\begin{aligned} &= 1.63 \text{ for } L=0.041 \text{ henry} \\ &0.45 \text{ for } L=0.0098 \text{ henry.} \end{aligned} \quad (37)$$

The measurement gives  $\left| \frac{V_{LR}}{V_C} \right| = 25.4/15.5 = 1.64$ . So the correct value for L is L=0.041 henry and the check is consistent.